
 


Lab 3 Simulations


Tri State buffer

 


T-type flip-flop




n-bit shift register

 


D flip-flop

 


n-bit register

 


n-bit register with load/~hold control

 


n-bit tri-state buffer

 

 
n-bit register load/~hold and tri-state output enable



 
n-bit shift register with parallel load input



4-bit linear feedback shift register

 

n-bit universal shift register

 

n-bit twisted ring counter

