
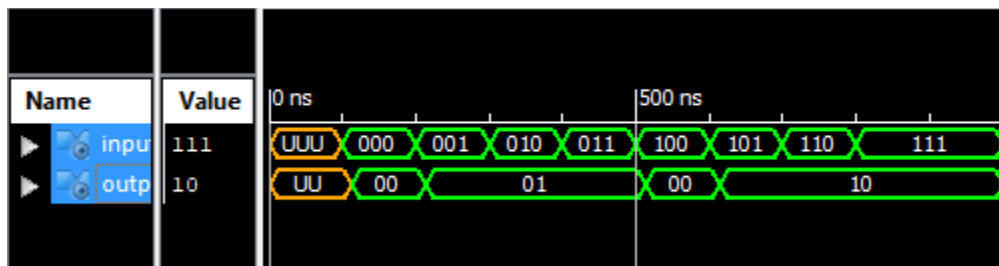



## Shift Control Logic

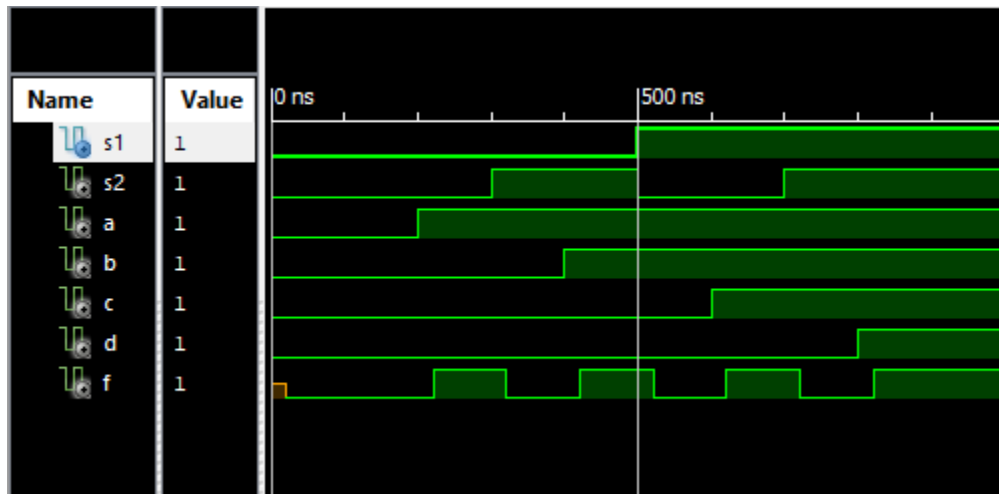


## 4 input mux




## One bit logicslice

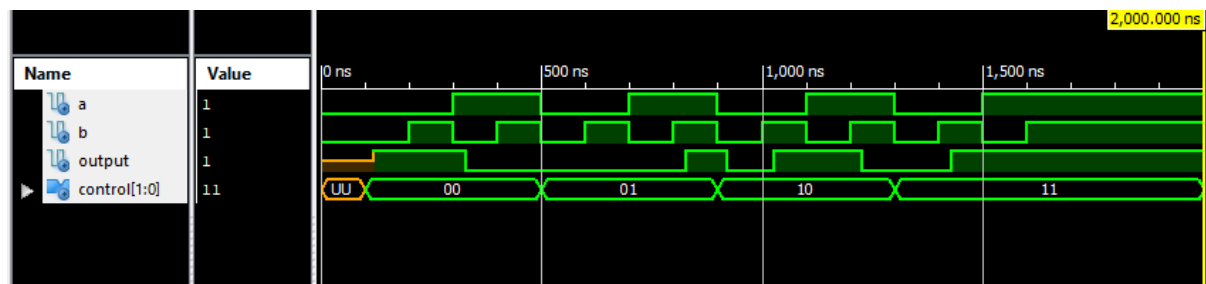


## Nbit adder

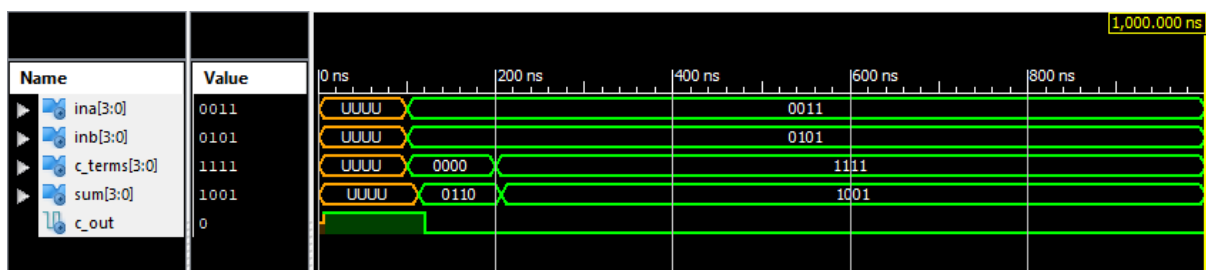

Fourbit lac adder

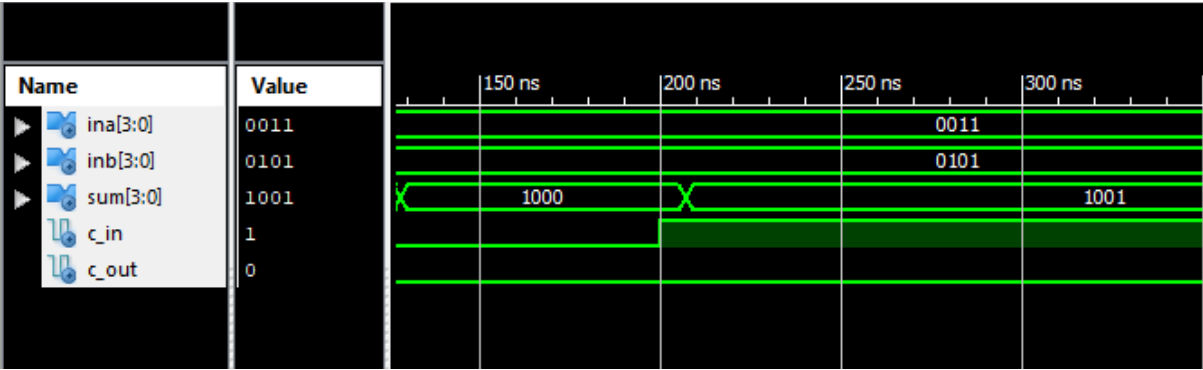


Nbit\_two\_input multiplexer

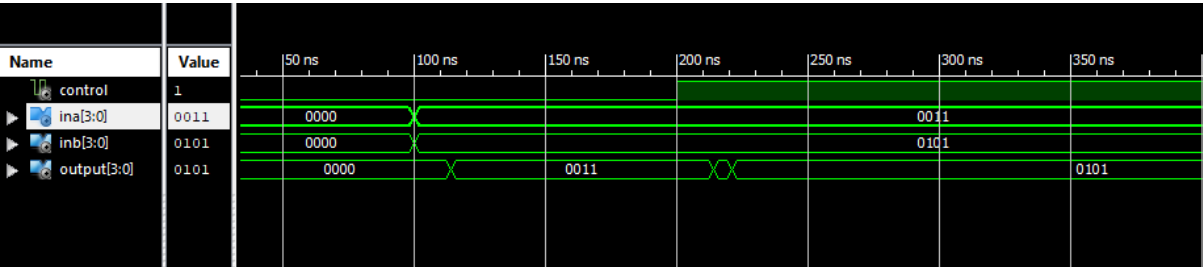


Nbit logic unit




Shift rotate

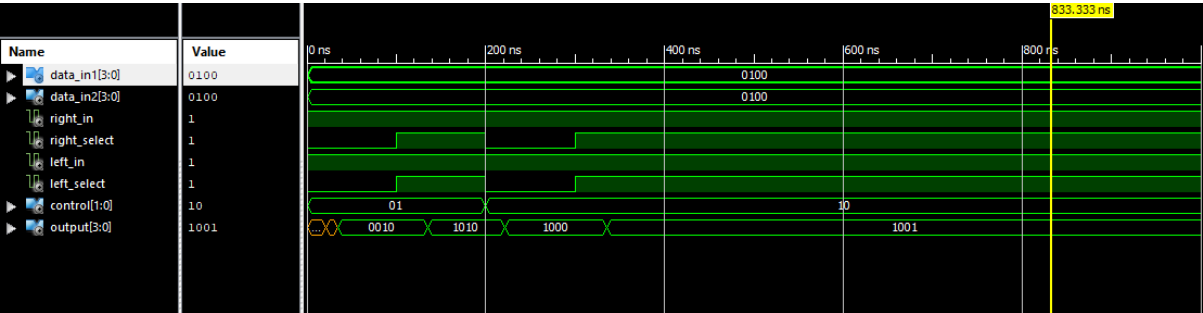




## Four bit lac adder

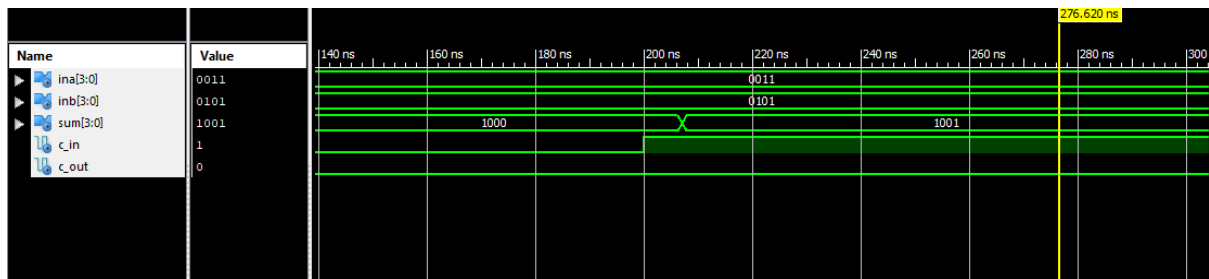

## Four bit adder subtractor

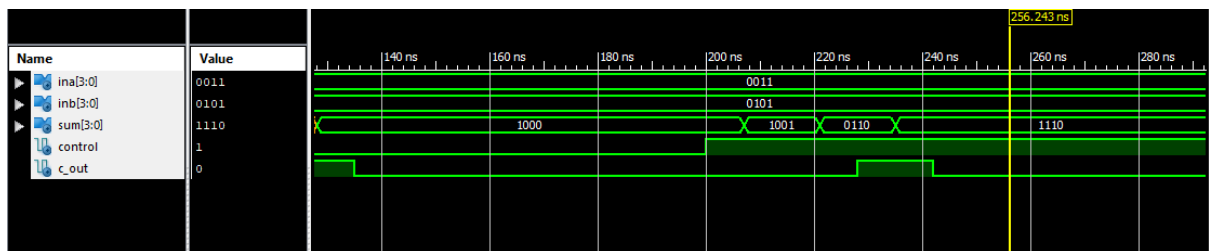

## Four bit arithmetic unit

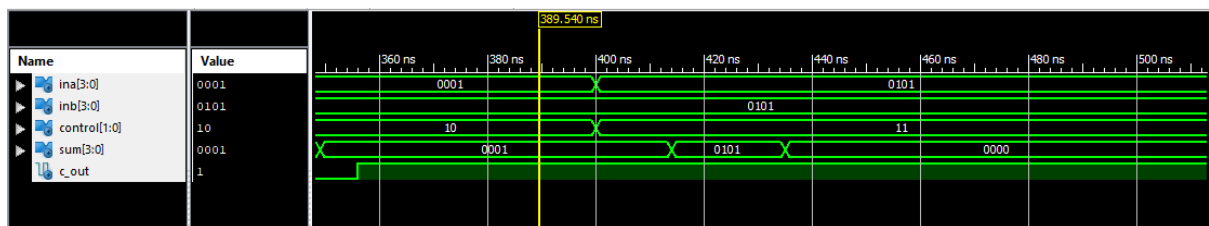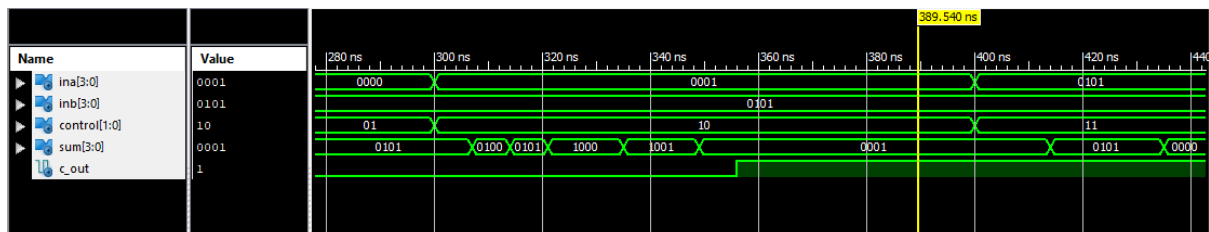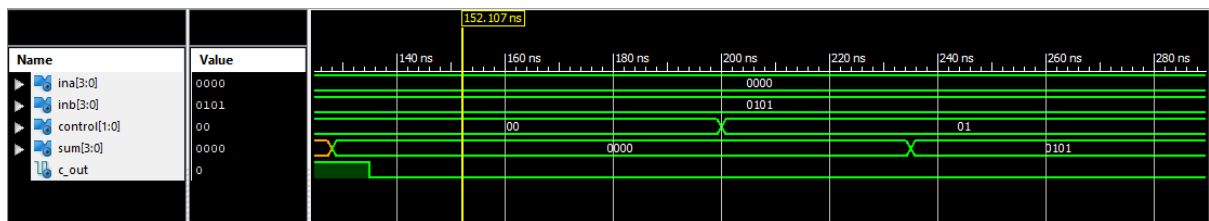

1. 4-bit ALU (top-level device)(code provided)
- 2.



3.

2. 4-bit Shifter (top-level device) (code provided)



